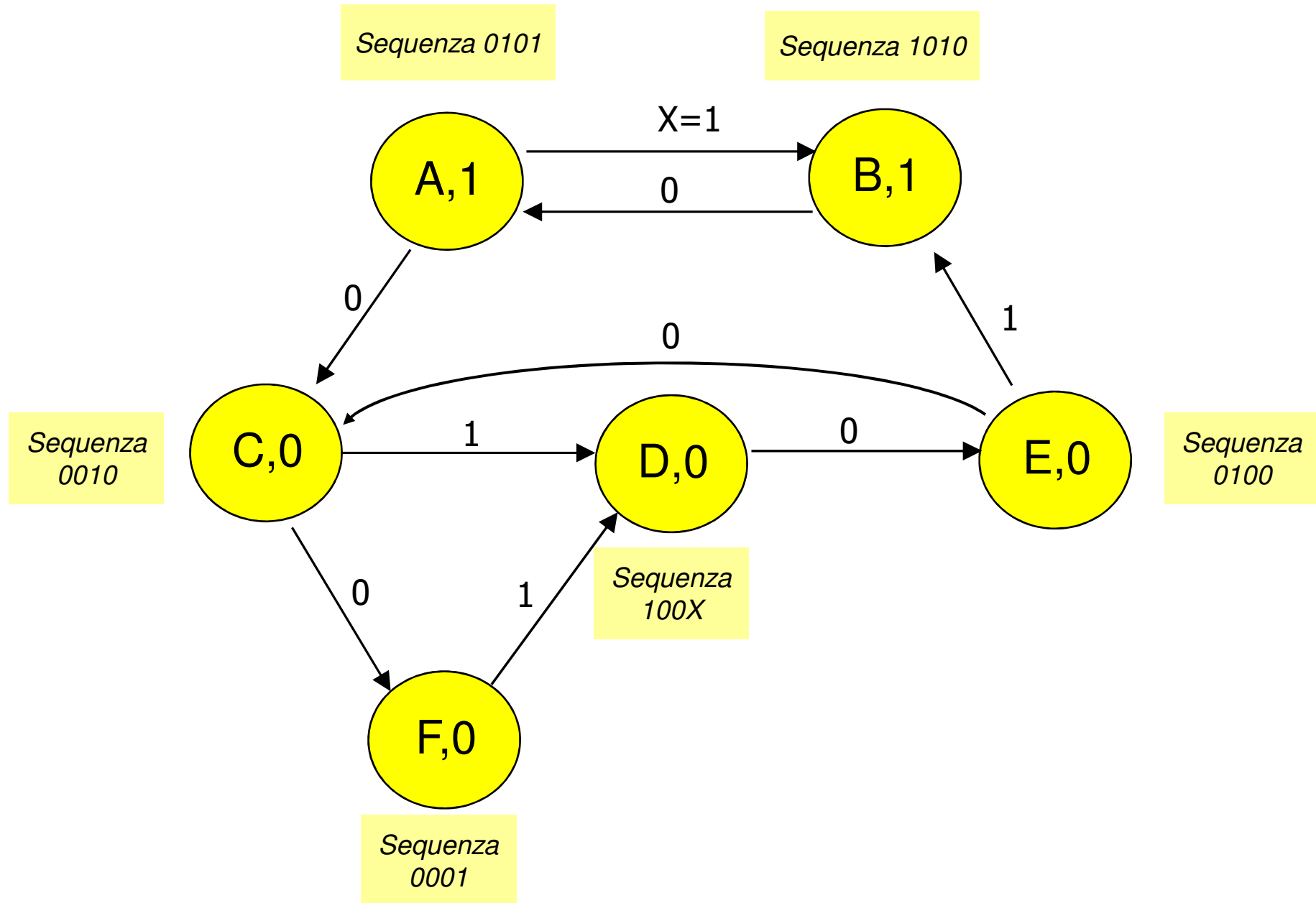


Esercizio 1.1 – Grafo



Esercizio 1.2 – TdF e TdT

		X		
		0	1	
s.p.	A	C	B	1
	B	A	-	1
	C	F	D	0
	D	E	-	0
	E	C	B	0
	F	-	D	0
		s.f.		Z

		X		
		0	1	
y₂y₁y₀	A=000	011	001	1
	B=001	000	---	1
	C=011	101	010	0
	D=010	100	---	0
	E=100	011	001	0
	F=101	---	010	0
	111	---	---	0
	110	---	---	-
			Y₂Y₁Y₀	


Esercizio 1.3 – Mappa variabile di peso minore

		Y_1Y_0			
		00	01	11	10
xy_2	00	1	0	1	0
	01	1	-	-	-
	11	1	0	-	-
	10	1	-	0	-


		Y_1Y_0			
		00	01	11	10
xy_2	00	1	1	0	0
	01	1	-	-	-
	11	0	0	-	-
	10	1	-	1	-

$$T_0 = y1' + x$$

Esercizio 1.4 – Sintesi con SR

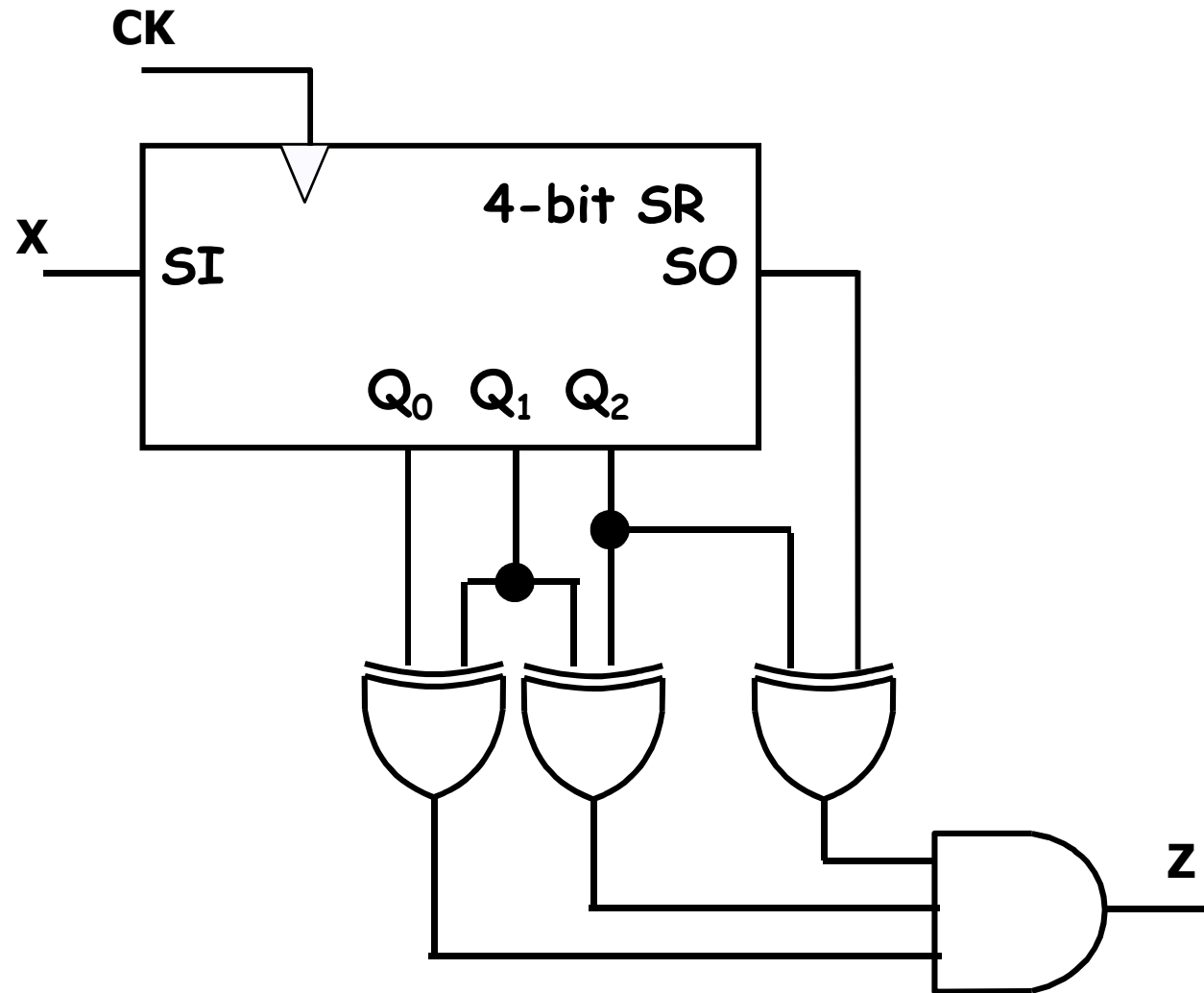

Esercizio 2.1 – Grafo primitivo

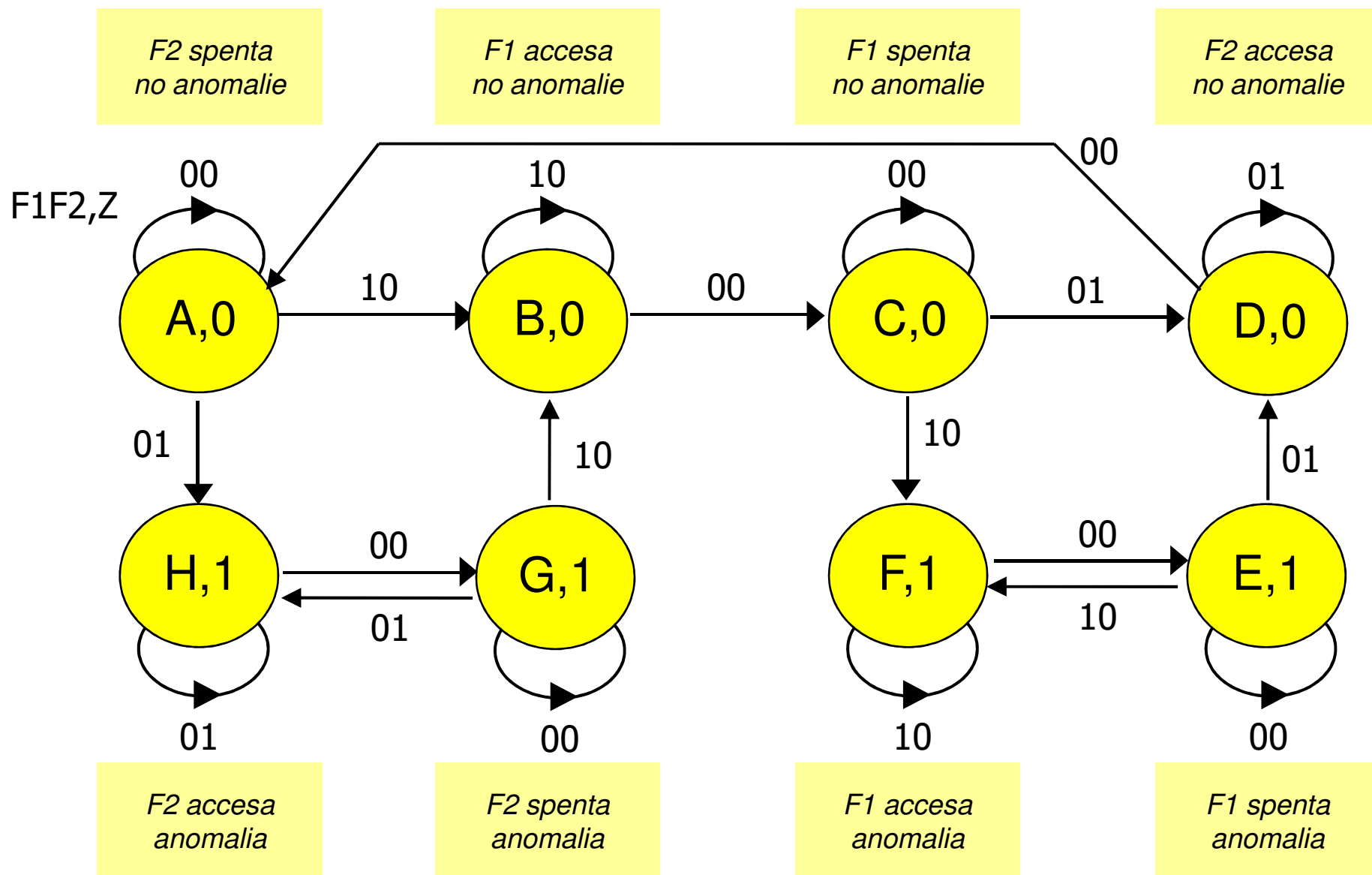

Esercizio 2.2 – Tabella triangolare e CMC


s.p.

		F1 F2			
		00	01	11	10
A	A,0	H,-	-, -	B,0	
B	C,0	-, -	-, -	B,0	
C	C,0	D,0	-, -	F,-	
D	A,0	D,0	-, -	-, -	
E	E,1	D,-	-, -	F,1	
F	E,1	-, -	-, -	F,1	
G	G,1	H,1	-, -	B,-	
H	G,1	H,1	-, -	-, -	

s.f., Z

B	AC						
C	DH BF	BF					
D	DH	AC	AC				
E							
F							
G					BF DH	BF EG	
H					EG DH	EG	
	A	B	C	D	E	F	G

A, B, C, D, EF, GH

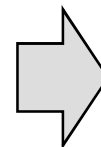


a={A}, b={B}, c={C},
d={D}, e={EF}, g={GH}

Esercizio 2.2 – TdF automa minimo

		F1 F2			
		00	01	11	10
s.p.	a	a,0	f,-	-, -	b,0
	b	c,0	-, -	-, -	b,0
	c	c,0	d,0	-, -	e,-
	d	a,0	d,0	-, -	-, -
	e	e,1	d,-	-, -	e,1
	f	f,1	f,1	-, -	b,-
		s.f., Z			

Esercizio 2.3 – Grafo adiacenze e TdT

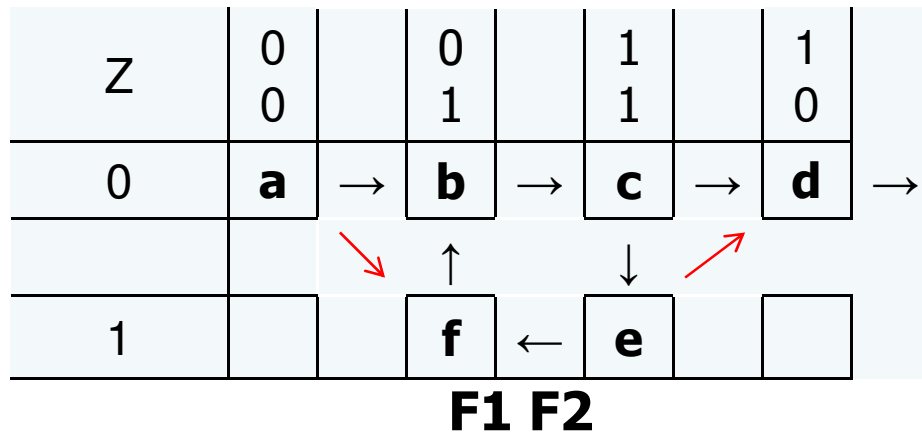

In giallo:
corse non critiche
modificando gli
s.f. per a ed e

	00	01	11	10
a = 000	000,0	001,-	-,-	001,0
b = 001	011,0	101,-	-,-	001,0
c = 011	011,0	010,0	-,-	111,-
d = 010	000,0	010,0	-,-	-,-
100	-,-	-,-	-,-	-,-
f = 101	101,1	101,1	-,-	001,-
e = 111	111,1	011,-	-,-	111,-
110	-,-	-,-	-,-	-,-

Y₂ Y₁ Y₀, Z

Esercizio 2.4 – Mappe per Y0

		F1 F2			
		00	01	11	10
y₁y₀	00	0	1	-	1
	01	1	1	-	1
	11	1	0	-	1
	10	0	0	-	-
		y₂ = 0			

		F1 F2			
		00	01	11	10
y₁y₀	00	-	-	-	-
	01	1	1	-	1
	11	1	1	-	1
	10	-	-	-	-
		y₂ = 1			

$$Y_0 = (y_1' + y_0) (y_1' + F_2' + y_2) (F_1 + F_2 + y_0)$$

Esercizio 2.4 – Mappe per Z

		F1 F2			
		00	01	11	10
$y_1 y_0$	00	0	-	-	0
	01	0	-	-	0
	11	0	0	-	-
	10	0	0	-	-

$y_2 = 0$

		F1 F2			
		00	01	11	10
$y_1 y_0$	00	-	-	-	-
	01	1	1	-	-
	11	1	-	-	-
	10	-	-	-	-

$y_2 = 1$

$$Z = y_2'$$

Esercizio 2.5 – Sintesi a NOR di Y0

$$Y_0 = (y1' + y0) (y1' + F2' + y2) (F1 + F2 + y0)$$

$$Y_0 = (y1' \downarrow y0) \downarrow (y1' \downarrow F2' \downarrow y2) \downarrow (F1 \downarrow F2 \downarrow y0)$$

